



Laboratory Report # 2

Name: Lauron, John Enrico D.

Date Completed: August 29, 2025

Laboratory Exercise Title: Basic Constructs in Verilog HDL

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 2B: Full Adder

In this exercise, we designed a 1-bit full adder using Verilog HDL with structural modeling and gate primitives. The circuit adds two inputs (x, y) and a carry-in (Cin) to produce the sum (S) and carry-out (Cout). Furthermore, the circuit was simulated using a testbench file to verify the generated waveform.

 


Figure 1. Entity Diagram of a Full Adder


I / O	Variable	Description
Inputs	A	First single-bit input
	B	Second single-bit input
	C_in	Carry-in
Outputs	C_out	Carry-out
	S	Sum

Table 1. Full Adder Circuit I/O




A	B	C_IN	S	C_OUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Table 2. Full Adder Circuit Truth Table

 

$$S = A \oplus B \oplus C_IN$$

Figure 2. K-Map of S Output

 

$$C_{out} = AB + C_{in} (A \oplus B)$$

Figure 3. K-Map of C_{out} Output

 


Figure 4. Full Adder Circuit Logic Diagram (with annotations)



Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat Aug 30 00:13:28 2025
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	FullAdder
Top-level Entity Name	FullAdder
Family	MAX 10
Device	10M50DCF484C7G
Timing Models	Final
Total logic elements	2
Total registers	0
Total pins	5
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Figure 5. Flow Summary of Full Adder

Type	ID	Message
Warning	18236	Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in your QSF to an appropriate value.
Information	20030	Parallel compilation is enabled and will use 4 of the 4 processors detected.
Information	12021	Found 1 design units, including 1 entities, in source file tb_halfadder.v
Information	12021	Found 1 design units, including 1 entities, in source file halfadder.v
Information	12021	Found 1 design units, including 1 entities, in source file fulladder.v
Information	12127	Elaborating entity "FullAdder" for the top level hierarchy
Information	12128	Elaborating entity "HalfAdder" for hierarchy "HalfAdder:HA1"
Information	286030	Timing-Driven Synthesis is running
Information	16010	Generating hard_block partition "hard_block:auto_generated_inst"
Information	21057	Implemented 7 device resources after synthesis - the final resource count might be different
Information		Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning

Figure 6. Synthesis Result of Full Adder

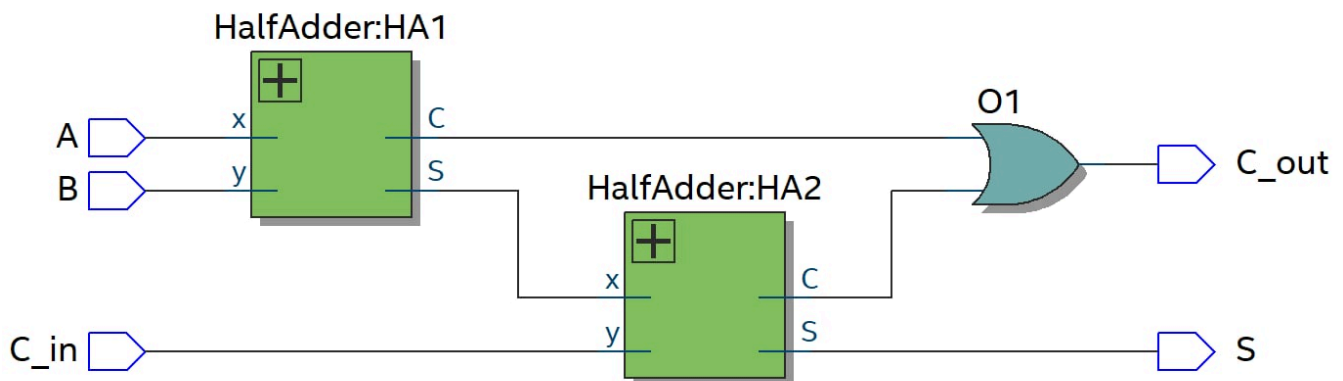


Figure 7. RTL View of Full Adder



```
FullAdder.v 267 268
1  /*****
2  * File:          FullAdder.v
3  * Author:       John Enrico Desalago Lauron
4  * Class:        CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description:  Verilog HDL Code of FullAdder
7  *****/
8
9  module FullAdder (A, B, C_in, S, C_out);
10
11      input  A, B, C_in;
12      output C_out, S;
13      wire  W1S, W2C, W3O;
14
15      HalfAdder HA1 (A, B, W2C, W1S);
16      HalfAdder HA2 (W1S, C_in, W3O, S);
17      or        O1  (C_out, W3O, W2C);
18
19  endmodule
20
```

Figure 8. Verilog HDL Code of Full Adder



```
FullAdder.v  Compilation Report - FullAdder  tb_FullAdder.v
1  /*****
2  * File:          tb_FullAdder.v
3  * Author:       John Enrico Desalago Lauron
4  * Class:       CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description:  Testbench file for FullAdder.v
7  *****/
8
9  `timescale 1 ns / 1 ps
10 module tb_FullAdder ();
11
12     reg    A, B, C_in;
13     wire   C_out, S;
14
15     FullAdder UUT (A, B, C_in, S, C_out);
16
17     initial
18     begin
19         A = 0; B = 0; C_in = 0;    #10
20         A = 0; B = 0; C_in = 1;    #10
21         A = 0; B = 1; C_in = 0;    #10
22         A = 0; B = 1; C_in = 1;    #10
23         A = 1; B = 0; C_in = 0;    #10
24         A = 1; B = 0; C_in = 1;    #10
25         A = 1; B = 1; C_in = 0;    #10
26         A = 1; B = 1; C_in = 1;    #30
27
28     $stop;
29     end
30 endmodule
31
32
```

Figure 9. Verilog HDL Code of Testbench Full Adder

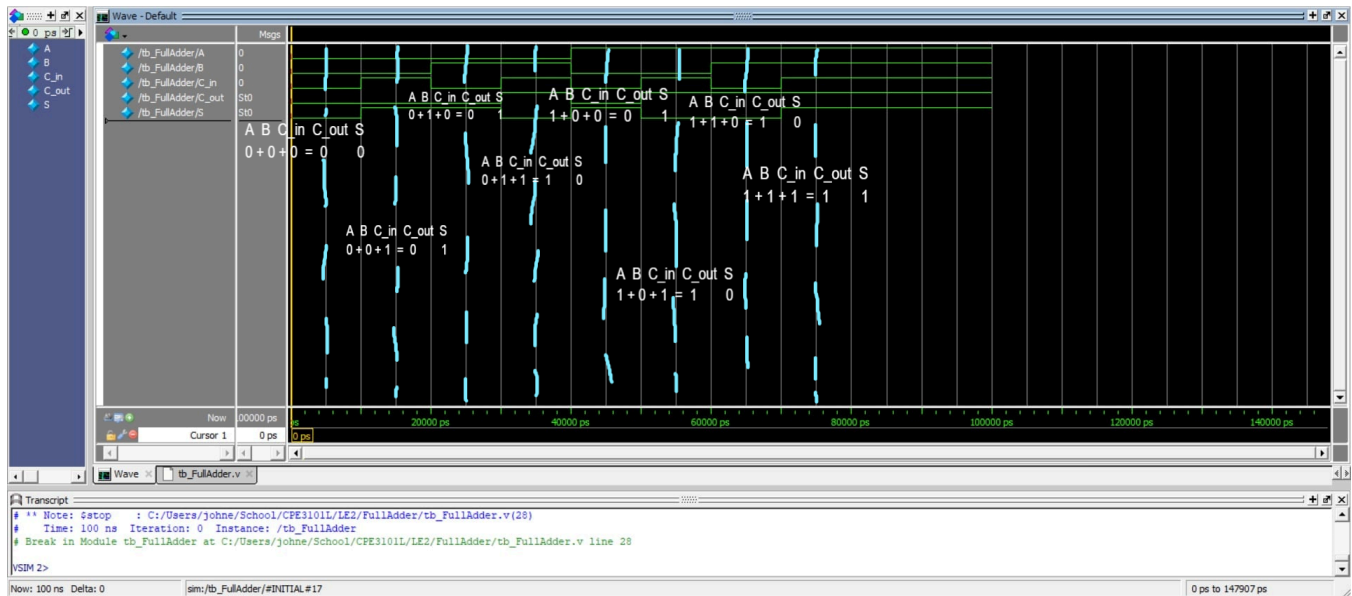


Figure 10. Testbench Waveform for Full Adder (with annotations)