



Laboratory Report # 3

Name: Lauron, John Enrico D.

Date Completed: September 5, 2025

Laboratory Exercise Title: Structural Modeling of Combinational Circuits

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 3A: 2x4 Decoder

In this exercise, we designed a 2-to-4 line decoder with an active-high enable (E) using Verilog HDL with structural modeling and gate primitives. The circuit decodes the 2-bit input (A) into four unique outputs (D) based on the enable signal. Furthermore, the design was synthesized and simulated using a testbench file to verify the correct output waveform.

 


Figure 1.Entity Diagram of 2x4 Decoder

Truth Table:

Inputs		Output
E	A	D
0	xx	0000
1	00	0001
1	01	0010
1	10	0100
1	11	1000

Table 1. Truth Table for 2x4 Decoder

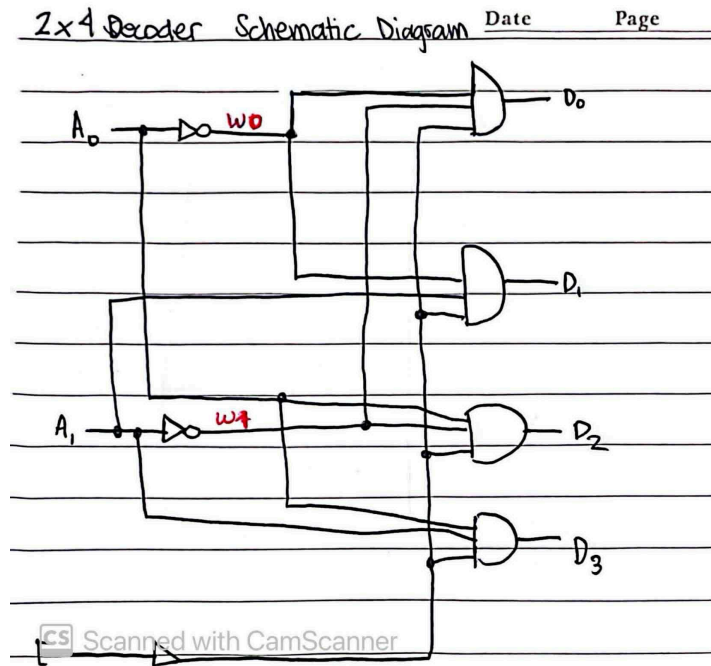


Figure 2. Schematic Diagram of a 2x4 Decoder

 


Figure 3. K-Maps for the 2x4 Decoder

Boolean Functions:

$$D_0 = A_0' A_1' \quad D_1 = A_0' A_1 \quad D_2 = A_0 A_1' \quad D_3 = A_0 A_1$$

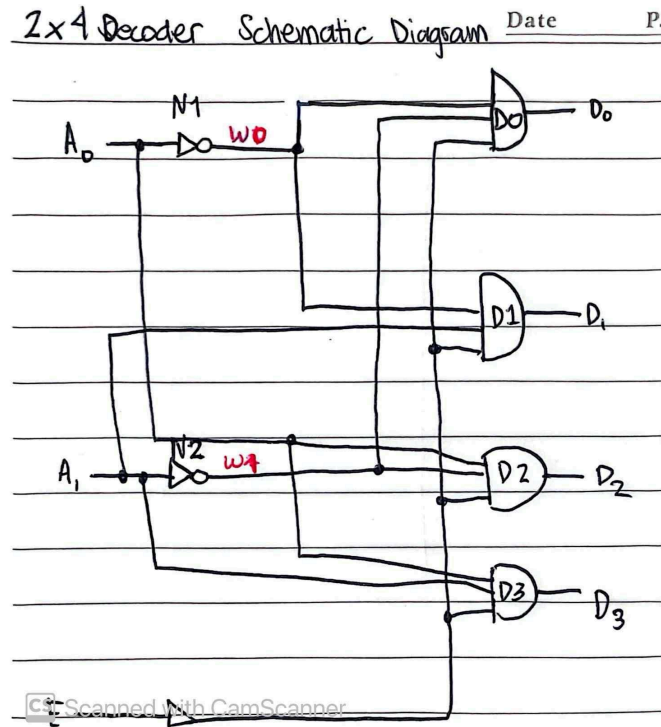


Figure 4. Circuit Diagram for 2x4 Decoder with Verilog HDL Labels

Flow Summary	
<<Filter>>	
Flow Status	Successful - Fri Sep 05 12:43:36 2025
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	Dec_2x4
Top-level Entity Name	Dec_2x4
Family	MAX 10
Device	10M50DCF484C7G
Timing Models	Final
Total logic elements	4
Total registers	0
Total pins	7
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Figure 5. Flow Summary of 2x4 Decoder



Type	ID	Message
		Running Quartus Prime Analysis & Synthesis
		Command: quartus_map --read_settings_files=on --write_settings_files=off Dec_2x4 -c Dec_2x4
	18236	Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in your QSF to an appropriate value for best performance.
	20030	Parallel compilation is enabled and will use 12 of the 12 processors detected
	12021	Found 1 design units, including 1 entities, in source file dec_2x4.v
	12127	Elaborating entity "Dec_2x4" for the top level hierarchy
	286030	Timing-Driven Synthesis is running
	16010	Generating hard_block partition "hard_block:auto_generated_inst"
	21057	Implemented 11 device resources after synthesis - the final resource count might be different
		Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning
		Running Quartus Prime Netlist Viewers Preprocess
		Command: quartus_rpp Dec_2x4 -c Dec_2x4 --netlist_type=gate
	18236	Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in your QSF to an appropriate value for best performance.
		Quartus Prime Netlist Viewers Preprocess was successful. 0 errors, 1 warning

Figure 6. Synthesis Result of 2x4 Decoder

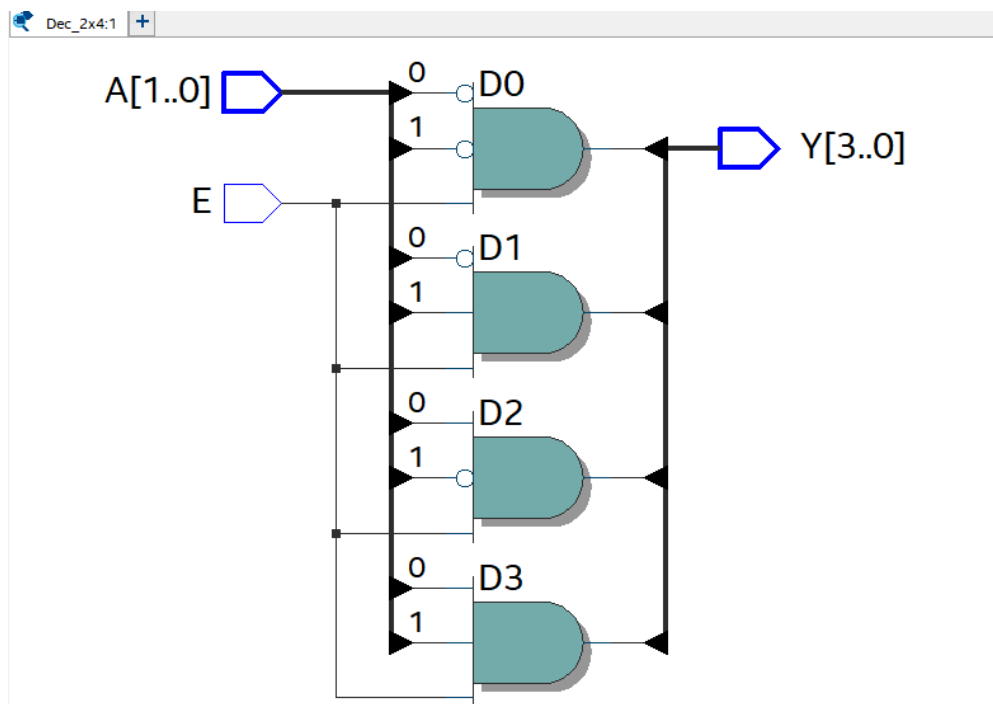


Figure 7. RTL View of 2x4 Decoder



```
Dec_2x4.v
1  /** *****
2  * File:          Dec_2x4.v
3  * Author:       John Enrico Desalago Lauron
4  * Class:        CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description:  Verilog HDL Code of a 2x4 Decoder
7  * *****/
8
9  // Structural Modeling of 2x4 Decoder
10 module Dec_2x4 (
11     input [1:0] A,
12     input      E,
13     output [3:0] Y
14 );
15
16     // Declare signals
17     wire [1:0] w;
18
19     // Implement with gate primitives
20     not N1 (w[0], A[0]);
21     not N2 (w[1], A[1]);
22
23     and D0 (Y[0], w[0], w[1], E);
24     and D1 (Y[1], w[0], A[1], E);
25     and D2 (Y[2], A[0], w[1], E);
26     and D3 (Y[3], A[0], A[1], E);
27
28 endmodule
29
30
```

Figure 8. Verilog HDL Code of a 2x4 Decoder



```
Dec_2x4.v  tb_Dec_2x4.v
1  /*****
2  * File:          tb_Dec_2x4.v
3  * Author:       John Enrico Desalago Lauron
4  * Class:        CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description:  Testbench file for Dec_2x4.v
7  *****/
8
9  `timescale 1 ns / 1 ps
10 module tb_Dec_2x4 ();
11
12     // Testbench signals
13     reg [1:0] A;
14     reg      E;
15     wire [3:0] Y;
16
17     // Instantiate the UUT
18     Dec_2x4 UUT(A, E, Y);
19
20     // generate stimuli
21     initial begin
22         $display ("Starting simulation at 0%ds.", $time);
23
24         E = 1'b0;    A = 2'b00;    #10
25                   A = 2'b01;    #10
26                   A = 2'b10;    #10
27                   A = 2'b11;    #10
28
29         E = 1'b1;    A = 2'b00;    #10
30                   A = 2'b01;    #10
31                   A = 2'b10;    #10
32                   A = 2'b11;    #10
33
34         $display ("Finished simulation at %0dns.", $time);
35
36         $stop;
37     end
38 endmodule
39
```

Figure 9. Verilog HDL Code of Testbench for a 2x4 Decoder

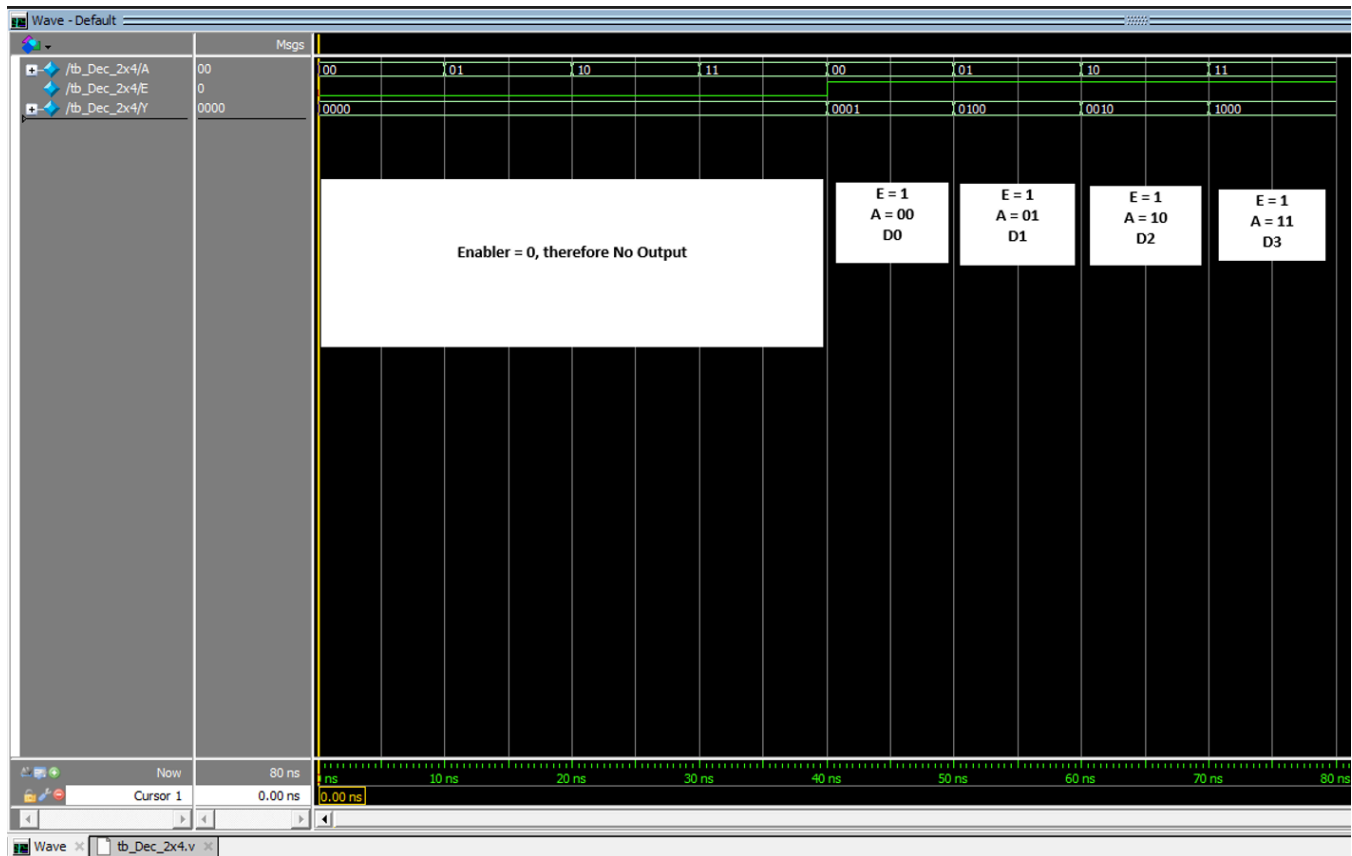


Figure 10. Testbench Waveform of a 2x4 Decoder (with annotations)

Exercise 3B: 4-bit Adder

In this exercise, we designed a 4-bit adder using Verilog HDL with structural modeling, based on the previously created full adder module. The circuit adds two 4-bit inputs (A and B) along with a carry-in (Cin) to generate a 4-bit sum (S) and a carry-out (Cout). Furthermore, the design was synthesized and simulated using a testbench file to confirm the functionality through waveform verification.

 


Figure 2. Entity Diagram of a 4-Bit Adder

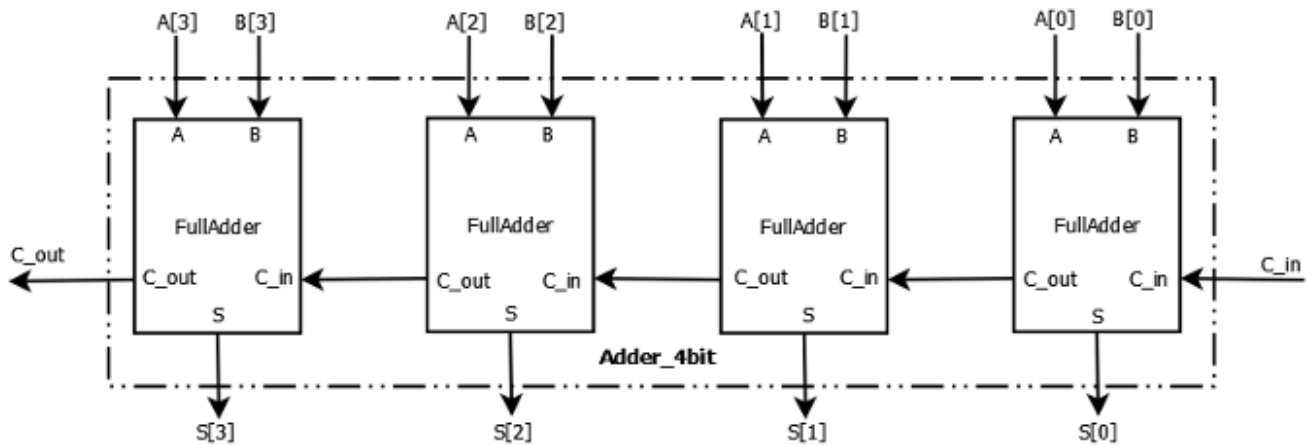


Figure 3. Structural Diagram of a 4-Bit Adder

Schematic Diagram of a 4-bit Adder using full-Adder

 


Figure 11. Circuit Diagram of a 4-bit Adder using Full-Adder with Verilog HDL Labels



Flow Summary	
<<Filter>>	
Flow Status	Successful - Fri Sep 05 18:33:56 2025
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	TopModule_4bit_Adder
Top-level Entity Name	TopModule_4bit_Adder
Family	MAX 10
Device	10M02DCU324A6G
Timing Models	Final
Total logic elements	8
Total registers	0
Total pins	14
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

Figure 12. Flow Summary of TopModule_4bit_Adder

```
Type | ID | Message
-----|-----|-----
> 1 Running Quartus Prime Analysis & Synthesis
> 1 Command: quartus_map --read_settings_files=on --write_settings_files=off TopModule_4bit_Adder -c TopModule_4bit_Adder
> 18236 Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in your QSF to an appropriate value for best performance.
> 20030 Parallel compilation is enabled and will use 12 of the 12 processors detected
> 12021 Found 1 design units, including 1 entities, in source file topmodule_4bit_adder.v
> 12021 Found 1 design units, including 1 entities, in source file /bs cpe 3rd year (1st sem)/cpe 31011/1e2/fulladder/fulladder.v
> 12021 Found 1 design units, including 1 entities, in source file /bs cpe 3rd year (1st sem)/cpe 31011/1e2/fulladder/halfadder.v
> 12021 Found 1 design units, including 1 entities, in source file /bs cpe 3rd year (1st sem)/cpe 31011/1e2/fulladder/tb_fulladder.v
> 12021 Found 1 design units, including 1 entities, in source file /bs cpe 3rd year (1st sem)/cpe 31011/1e2/fulladder/tb_halfadder.v
> 12127 Elaborating entity "TopModule_4bit_Adder" for the top level hierarchy
> 12128 Elaborating entity "FullAdder" for hierarchy "FullAdder:F1"
> 12128 Elaborating entity "HalfAdder" for hierarchy "FullAdder:F1|HalfAdder:HA1"
> 286030 Timing-Driven Synthesis is running
> 16010 Generating hard_block partition "hard_block:auto_generated_inst"
> 21057 Implemented 22 device resources after synthesis - the final resource count might be different
> 1 Quartus Prime Analysis & synthesis was successful. 0 errors, 1 warning
```

Figure 13. Synthesis Result of TopModule_4bit_Adder

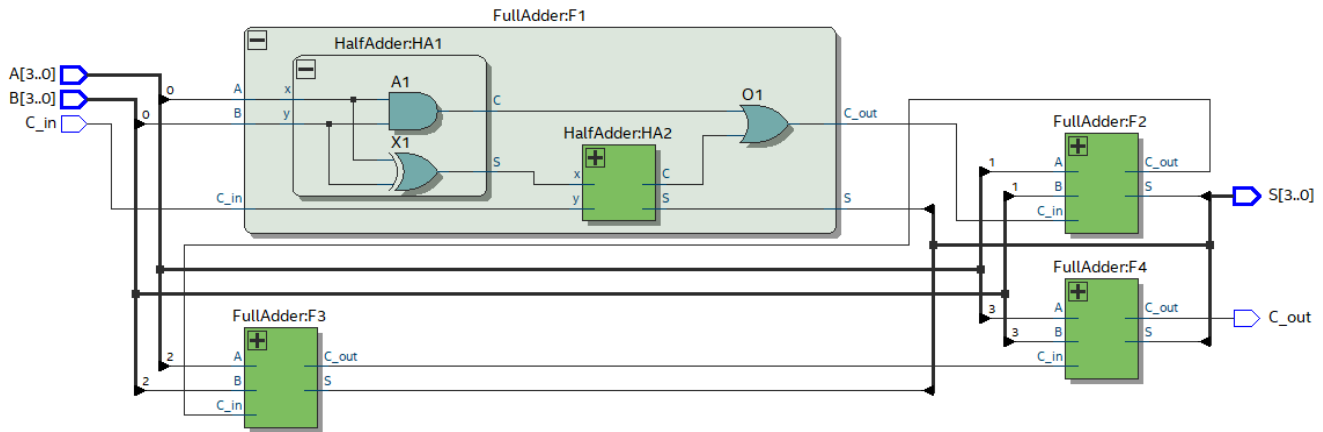


Figure 14. RTL View of TopModule_4bit_Adder

```
TopModule_4bit_Adder.v  FullAdder.v  HalfAdder.v  Compilation Report - TopModule_4bit_Adder
1  ****
2  * File: TopModule_4bit_Adder.v
3  * Author: John Enrico Desalago Lauron
4  * Class: CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description: Verilog HDL Code of a 4-bit Adder using Full-Adder
7  ****
8  // Structural Modeling of 4-bit Ripple Carry Adder
9  module TopModule_4bit_Adder (
10     input [3:0] A,
11     input [3:0] B,
12     input C_in,
13     output [3:0] S_out,
14     output [3:0] S
15 );
16     // Declare signals
17     wire [2:0] w;
18
19     // Instantiate First Full Adder (LSB)
20     FullAdder F1(
21         .A(A[0]),
22         .B(B[0]),
23         .C_in(C_in),
24         .C_out(w[0]),
25         .S(S[0])
26     );
27
28     // Instantiate Second Full Adder
29     FullAdder F2(
30         .A(A[1]),
31         .B(B[1]),
32         .C_in(w[0]),
33         .C_out(w[1]),
34         .S(S[1])
35     );
36
37     // Instantiate Third Full Adder
38     FullAdder F3(
39         .A(A[2]),
40         .B(B[2]),
41         .C_in(w[1]),
42         .C_out(w[2]),
43         .S(S[2])
44     );
45
46     // Instantiate Fourth Full Adder (MSB)
47     FullAdder F4(
48         .A(A[3]),
49         .B(B[3]),
50         .C_in(w[2]),
51         .C_out(C_out),
52         .S(S[3])
53     );
54 endmodule
```

Figure 15. Verilog HDL Code of TopModule_4bit_Adder



```
TopModule_4bit_Adder.v FullAdder.v HalfAdder.v tb_TopModule_4bit_Adder.v Compilation Report - TopModule_4bit_Adder.v
3  * Author: John Enrico Desalago Lauron
4  * Class: CPE 3101L
5  * Group/Schedule: Group 1 Fri 7:30 - 10:30 AM
6  * Description: Testbench for TopModule_4bit_Adder.v
7  * *****/
8
9  `timescale 1 ns / 1 ps
10
11  // Testbench Module
12  module tb_TopModule_4bit_Adder;
13
14  // Declare Testbench signals
15  reg [3:0] A;
16  reg [3:0] B;
17  reg C_in;
18  wire [3:0] S;
19  wire C_out;
20
21  // Instantiate the UUT
22  TopModule_4bit_Adder UUT (
23      .A (A),
24      .B (B),
25      .C_in (C_in),
26      .S (S),
27      .C_out (C_out)
28  );
29
30  // generate stimuli
31  initial begin
32      // Display header in simulation log
33      $display("Time\tA\tB\tC_in\tS\tC_out");
34      $display("-----");
35
36      // Apply another 8 input combinations
37      A = 4'b0100; B = 4'b0010; C_in = 0; #10;
38      A = 4'b0110; B = 4'b0011; C_in = 1; #10;
39      A = 4'b1001; B = 4'b0100; C_in = 0; #10;
40      A = 4'b0111; B = 4'b1000; C_in = 1; #10;
41      A = 4'b1011; B = 4'b0110; C_in = 0; #10;
42      A = 4'b1100; B = 4'b1100; C_in = 1; #10;
43      A = 4'b1000; B = 4'b1000; C_in = 0; #10;
44      A = 4'b0110; B = 4'b0110; C_in = 1; #10;
45
46      // End simulation
47      $stop;
48  end
49
50  // Monitor signal changes
51  initial begin
52      $monitor("%0dns\t%b\t%b\t%b\t%b\t%b",
53              $time, A, B, C_in, S, C_out);
54  end
55
56  endmodule
```

Figure 16. Testbench Verilog HDL Code of TopModule_4bit_Adder

```
# run -all
# Time A B C_in S C_out
# -----
# 0ns 0000 0000 0 | 0000 0
# 10ns 0001 0010 0 | 0011 0
# 20ns 0011 0011 1 | 0111 0
# 30ns 0101 0011 0 | 1000 0
# 40ns 1111 0001 0 | 0000 1
# 50ns 1010 0101 1 | 0000 1
# 60ns 1111 1111 0 | 1110 1
# 70ns 1111 1111 1 | 1111 1
# ** Note: $stop : D:/BS CpE 3rd Year (1st Sem)/CPE 3101L/LE3/3B/tb_TopModule_4bit_Adder.v(47)
# Time: 80 ns Iteration: 0 Instance: /tb_TopModule_4bit_Adder
# Break in Module tb_TopModule_4bit_Adder at D:/BS CpE 3rd Year (1st Sem)/CPE 3101L/LE3/3B/tb_TopModule_4bit_Adder.v line 47
```

Figure 17. Transcript for the Testbench Output

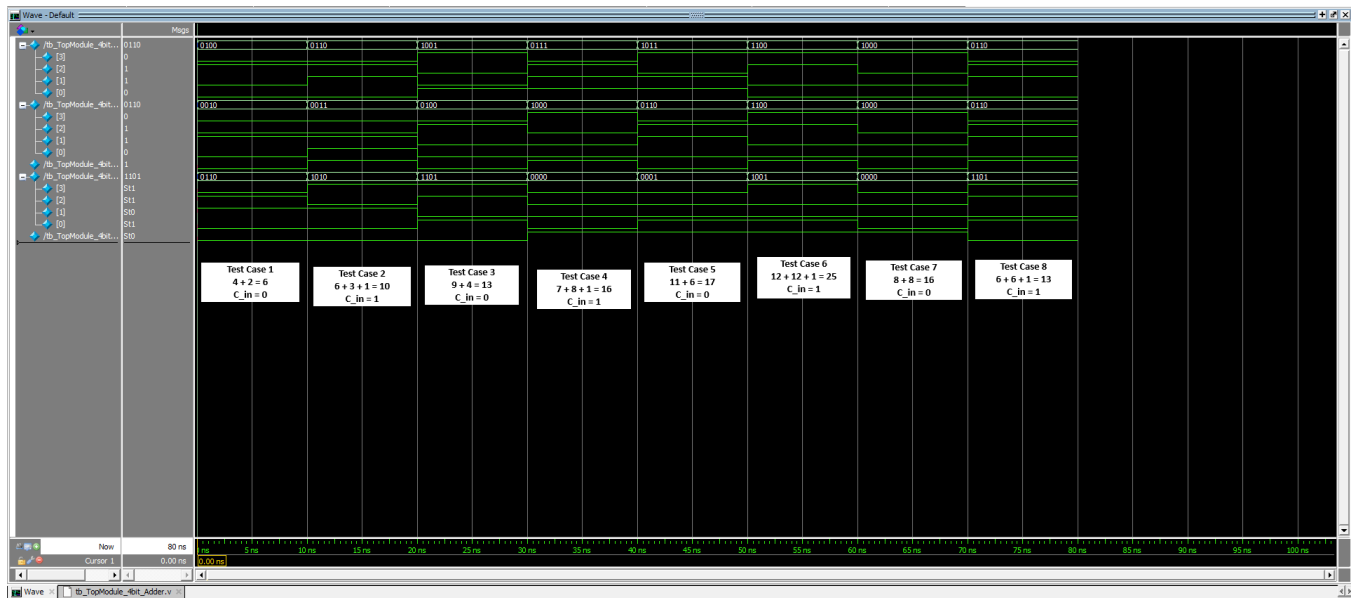


Figure 18. Testbench Waveform of TopModule_4bit_Adder (with annotations)